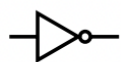


## 2. Logic gates and logic circuits

### 3.2 Logic Gates and Logic Circuits

Candidates should be able to:

Use the following logic gate symbols:



NOT



AND



OR



NAND



NOR



XOR

Understand and define the functions of :

NOT, AND, OR, NAND, NOR and XOR (EOR) gates

Construct the truth table for each of the logic gates above

Construct a logic circuit

Construct a truth table

Construct a logic expression

Notes and guidance

All gates except the NOT gate will have two inputs only.

From:


- a problem statement
- a logic expression
- a truth table

From:


- a problem statement
- a logic circuit
- a logic expression

From:

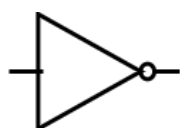
- a problem statement
- a logic circuit
- a truth table




NOT

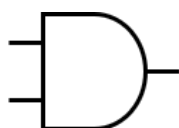


AND

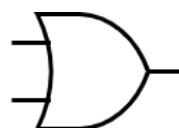

OR

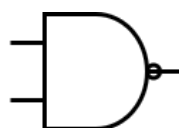

NAND

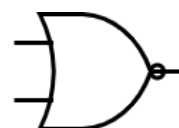

NOR



XOR

## Truth tables

- NOT

A	X
0	1

A	X
1	0

- AND

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

- OR

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

- NAND

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

- NOR

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

- XOR

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0